

## **Kanga US**

3521 Spring Lake Dr.  
Findlay, OH 45840-9073  
[kanga@kangaus.com](mailto:kanga@kangaus.com)  
[www.kangaus.com](http://www.kangaus.com)

May 9, 2009

The Improved microR1 receiver “kitlet” is a bag of parts that contains all the electronic parts you will need to build the Improved microR1 Receiver. This circuit started out on pages 8.4 – 8.6 of Experimental Methods in RF Design. KK7B has used the circuit as a lab project in classes he has taught, and over time several improvements have come about.

There is no printed circuit board for the kitlet. Build it ugly style on a piece of copper clad.

Documentation for this project is minimal. Refer to EMRFD and the notes included with the kitlet for more info on the circuit. You will find that the Double Tuned Circuit in the front end of the Improved uR1 does not have the components specified in the notes with the Kitlet. It says to “select them for the frequency of interest”. You can put the Improved microR1 on any of the HF bands by using the appropriate crystal and front end double tuned circuit.

The kitlet comes supplied with a 40 meter crystal and front end DTC components. The inductors are wound on the T50-2 toroids (red) - 20 turns for the main winding on each toroid with a 5 turn link winding on each toroid. The top coupling capacitor is a 20 pf trimmer (green) the capacitor across each inductor is actually made up of two capacitors in parallel – a 50 pf trimmer (green) in parallel with a 180 pf disc cap..

Have fun!


73 – Bill – N8ET  
Kanga US

# Simple Improvements to a Simple Receiver


Rick Campbell 24 April 2008

The simple receiver circuit presented on pages 8.4 - 8.6 of EMRFD has been widely duplicated and used as a starting point for many experiments. As with any receiver design intended to be built using available components, each version is different. A recent exercise resulted in several improvements to the ugly constructed receiver in the photograph in the upper left corner of page 8.4.

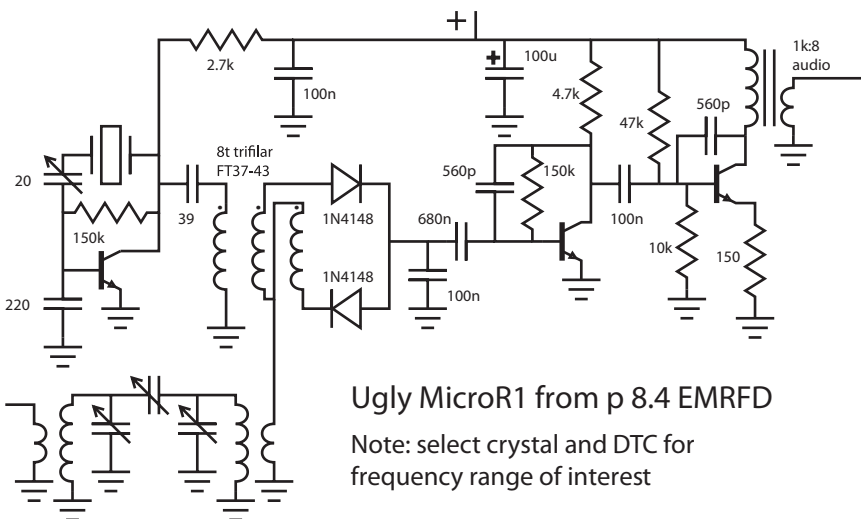This is the actual schematic diagram of the receiver in the photograph. It differs slightly from the schematic in the book, but is essentially as described in the text. Critical listening revealed weak audio, as expected, and lots of high frequency noise and signals. When operated using a bench supply instead of a 9v battery, there was some tunable hum.




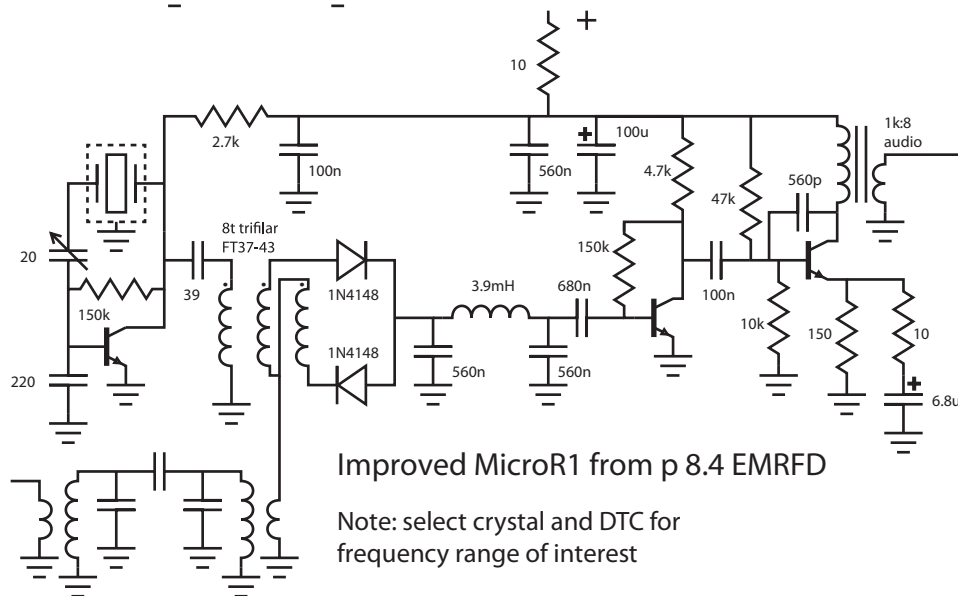The minor changes to the circuit may be seen in the schematic to the right. A simple low pass filter restricts the audio frequency response to a range useful for CW and SSB. The 560pF capacitor was removed from the first transistor audio stage, because it didn't seem to do much.



Restricting the audio bandwidth allows more gain, so the AC emitter bypass was added to the output stage. Additional power supply decoupling eliminated most of the tunable hum, and soldering a short wire from the crystal can to ground eliminated the rest. After tuning the input double tuned circuit, the variable capacitors were removed, measured, and replaced with fixed capacitors. This permits a more compact layout. The final receiver is built ugly style on a 1.3" by 3.2" board, and is delightful to listen to.

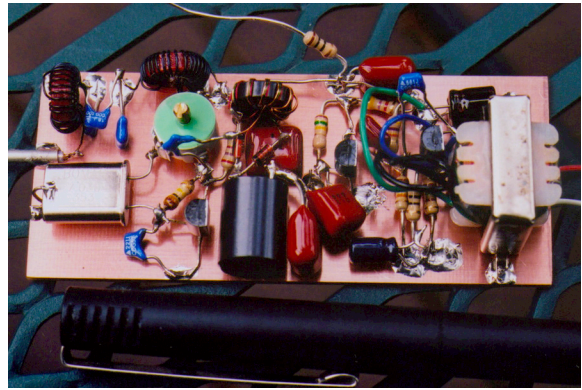Here is a photo of the completed receiver in its natural environment, sitting on the backyard picnic table. A Uniball pen is for scale comparison. The receiver is simple, small, and draws 8 mA from a 9 volt battery, but hears signals from thousands of miles away when connected to a half-wave dipole antenna 30 feet up.



Here is a detail shot of the RF, LO, and mixer. The mixer in this application is often called a "Product Detector." The antenna input is the small coax soldered to the board at the left. The simple Pierce oscillator with 7.030 MHz crystal and green trimmer capacitor are on the lower left part of the board. The product detector with its trifilar toroid, two diodes, and bypass capacitor are in the upper right. The audio low-pass inductor is the gray cylinder on the bottom right.

Here is the detail shot of the product detector and audio section. The gain is low enough that there is no need for a volume control, even though the band noise is clearly audible in the headphones. One simple way to implement a volume control would be a 100 ohm variable resistor directly across the headphone jack. That varies gain by reducing RL for the output stage.



<b>Improved microR1 Parts List</b>			
<b>Part</b>	<b>Value</b>	<b>Digikey</b>	<b>Mouser</b>
C1A	50p trim	SG3009-ND	
C1B	180p		140-50P2-181
C2	20p trim	SG3003-ND	
C3A	50p trim	SG3009-ND	
C3B	180p		140-50P2-181
C4	220p		140-50P2-221
C5	20p trim	SG3003-ND	
C6	39p		140-50N2-390
C7	100n	P4525-ND	
C8	560n	P4672-ND	
C9	560n	P4672-ND	
C10	680n	P4673-ND	
C11	560n	P4672-ND	
C12	100u	P833-ND	
C13	100n	P4525-ND	
C14	560p		140-50P2-561
L1	3.9 mh		434-02-392j
C15	6.8u	P909-ND	
R1	150k	150kqbk-nd	
R2	2.7k	2.7kqbk-nd	
R3	150k	150kqbk-nd	
R4	4.7k	4.7kqbk-nd	
R5	47k	47kqbk-nd	
R6	10k	10kqbk-nd	
R7	150 ohms	150qbk-nd	
R8	10 ohms	10qbk-nd	
R9	10 ohms	10qbk-nd	
T1	T50-2	20T : 5T	
T2	T50-2	20T : 5T	
T3	FT37-43	8T Trifilar	
T4	1k:8		42TM003-RC
TR1	2N3904		512-2N3904T
TR2	2N3904		512-2N3904T
TR3	2N3904		512-2N3904T
CR1	1N4148		512-1N4148T
CR2	1N4148		512-1N4148T
xtal	7.030 MHz		
stereo jack		CP1-3531N-N	161-3402E